



SN – 390

I Semester B.Sc. Examination, November/December 2017
(CBCS) (2014 – 15 and Onwards) (F+R)
ELECTRONICS – I
Basic Electronics

Time : 3 Hours

Max. Marks : 70

Note : 1) Answer **all** questions from Part – A, **any five** from Part – B
and **any four** questions from Part – C.

2) Answer **all** questions from Part – A in **any one** page, the
same question answered multiple times will **not** be
considered for evaluation.

PART – A

Answer **all** the sub divisions.


(15×1=15)

1. i) We need a resistor of value $47\text{ K}\Omega$ with $\pm 5\%$ tolerance. The sequence of the color band on this resistor should be
 - a) yellow, violet, yellow and gold
 - b) yellow, violet, orange and gold
 - c) yellow, violet, orange and silver
 - d) yellow, violet, brown and gold
- ii) In a step up transformer, the number of turns in the secondary coil is
 - a) Less than primary coil turns
 - b) More than primary coil turns
 - c) Equal to primary coil turns
 - d) None of the above
- iii) Thevenin's equivalent circuit consists of a
 - a) constant voltage source with a resistance in parallel
 - b) constant voltage source with a resistance in series
 - c) a current source with an voltage source
 - d) current source in series with a resistance
- iv) According to Kirchhoff's current law, the algebraic sum of the currents meeting at a point is always
 - a) zero
 - b) positive
 - c) negative
 - d) equal to unity
- v) In order to obtain a maximum power from the terminals of a network, the load resistance should be
 - a) greater than the circuit resistance
 - b) equal to the circuit resistance
 - c) less than the circuit resistance
 - d) double the circuit resistance

P.T.O.



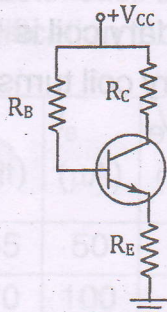- vi) Current flows through a Germanium practical diode when the forward bias applied to it exceeds
- 0.3 v
 - 1 v
 - 0.7 v
 - 0 volt
- vii) Third approximation of a diode is represented by
- only a dc source
 - dc source with a series resistance
 - dc source with a series resistance and an ideal diode
 - a dc source parallel with a resistance
- viii) Theoretical value of ripple factor for a Center Tap Full Wave Rectifier is
- 0.482
 - 0.812
 - 1.11
 - 1.21
- ix) In voltage regulator circuits, Zener diode is operated in
- forward bias mode
 - forward breakdown region
 - reverse breakdown region
 - none of the above
- x) Transistor acts as a switch in
- cut off and saturation regions
 - cut off and active regions
 - saturation and active regions
 - in all the three regions
- xi)



The circuit shown above is

- Fixed bias
 - Fixed bias with emitter feedback
 - Collector to base bias
 - Voltage divider bias
- xii) In an N Channel Field-Effect Transistor (FET), the gate is
- a P type semiconductor
 - a N type semiconductor
 - both a and b
 - none of the above
- xiii) The code used in digital systems to represent decimal digits, alphabets and other special characters such as +, -, *, etc. is
- Hexadecimal
 - Octal
 - BCD
 - ASCII



- xiv) The principal characteristic feature of gray code is
- It changes by only one bit between two consecutive numbers
 - It has more number of ones
 - It has more number of zeros
 - It changes by two bits between two consecutive numbers
- xv) Invalid numbers in BCD are
- 1001, 1000, 0111, 0000, 0010 and 0011
 - 0001, 0010, 0111, 0110, 0010 and 0011
 - 1010, 1011, 1100, 1101, 1110 and 1111
 - 1000, 1001, 0111, 0010, 0011 and 0111

PART - B

Answer **any five** questions.

(5×7=35)


- Explain the method of conversion of a voltage source into a current source.
 - Draw the circuit diagram of series RC circuit. Write the expressions for charging and discharging of the circuit. Show it graphically. (2+5)
- Draw a series RL circuit excited by an a.c. source. Write the equations for voltage, impedance and phase angle.
 - Draw the circuit symbols for SPDT, DPDT and SPST switches. (4+3)
- State Maximum power transfer theorem.
 - State Norton's theorem. With suitable circuit diagrams, explain the steps to Nortonise a resistive network. (2+5)
- Draw the circuit diagram of full wave bridge rectifier and explain its working. Draw the input and output wave forms. Mention its advantages and disadvantages. 7
- What is a filter ? Draw the circuit diagram of capacitor filter.
 - With the circuit diagram, explain working of Zener diode voltage regulator. (2+5)
- Define α and β of a transistor.
 - Draw the experimental circuit to study CE characteristics of a transistor. Plot the input and output characteristics graphs and indicate the different regions. (2+5)
- Draw the diagram of voltage divider biasing circuit. Write the expressions for Q point.
 - With necessary diagram, explain the working of JFET. (3+4)
- Explain with numerical example, method to convert a decimal number into its binary equivalent. Consider the integer and fractional parts of decimal number.
 - Write the BCD and Excess 3 code for all the decimal digits. (4+3)



PART – C

Answer **any four** questions.**(4×5=20)**

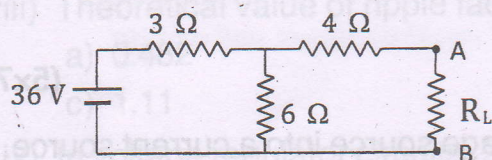10. A series resonance circuit has a capacitor of 100 pF, an inductor of 100 μ H and a resistor of 5 Ω . Calculate.
- Resonant frequency
 - Band width when Q factor is 200.
11. Using Thevenin's theorem, find the current in $R_L = 10 \Omega$ in the following circuit. Also write Thevenin's equivalent circuit.



12. Calculate efficiency and PIV of a half wave rectifier circuit with an input voltage of 220 V rms and load R_L of 100 Ω . Given $r_d = 5 \Omega$ and turns ratio of the transformer is 10 : 1.
13. Following observations have been recorded in an experiment to plot the characteristics of an NPN transistor in CE mode. Determine, r_i , r_o and the current amplification factor β_{ac} .

V_{BE} (volt)	I_B (μ A)	V_{CE} (volt)	I_C (mA)
0.65	50	6	5
0.70	100	6	10
0.70	100	11	10.5

14. Subtract the following numbers using 2's complement method

i) $(BF)_{16} - (FB)_{16}$

ii) $(10010)_2 - (1001)_2$

(3+2)

15. a) Convert the following Gray numbers in to equivalent binary numbers.

i) 1001010

ii) 11001100

b) Express the $(F5)_{16}$ in binary and decimal number.

(3+2)